


# Übungen zur TI

2. Übung


# Inhalt

- Transistor
- AND-Gate
- NAND, NOR, XOR, AND, OR, X
- Logic Gates as NAND
- Übung Binärzähler Tabellenkalkulation
- Domino, Lego, Minecraft Computer
- Hausaufgabe Binärzähler


# Transistor

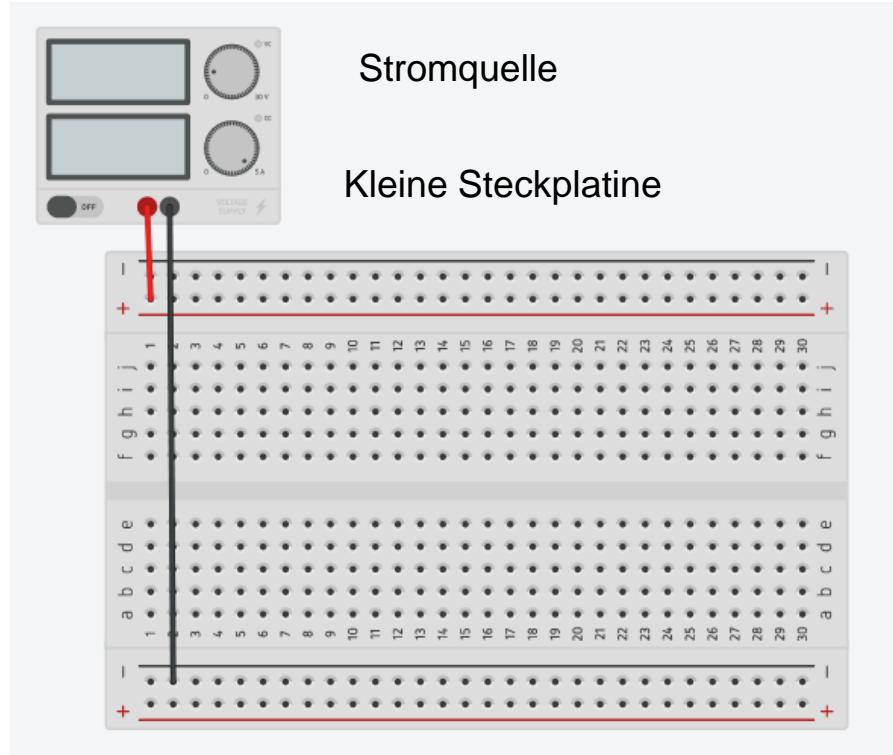


# Transistor

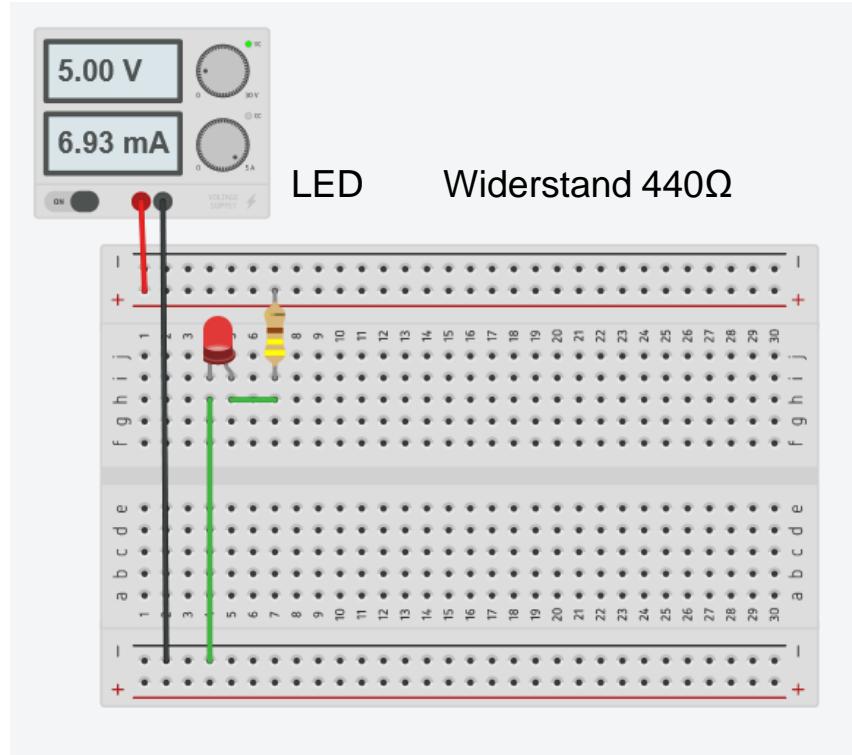



# Transistor

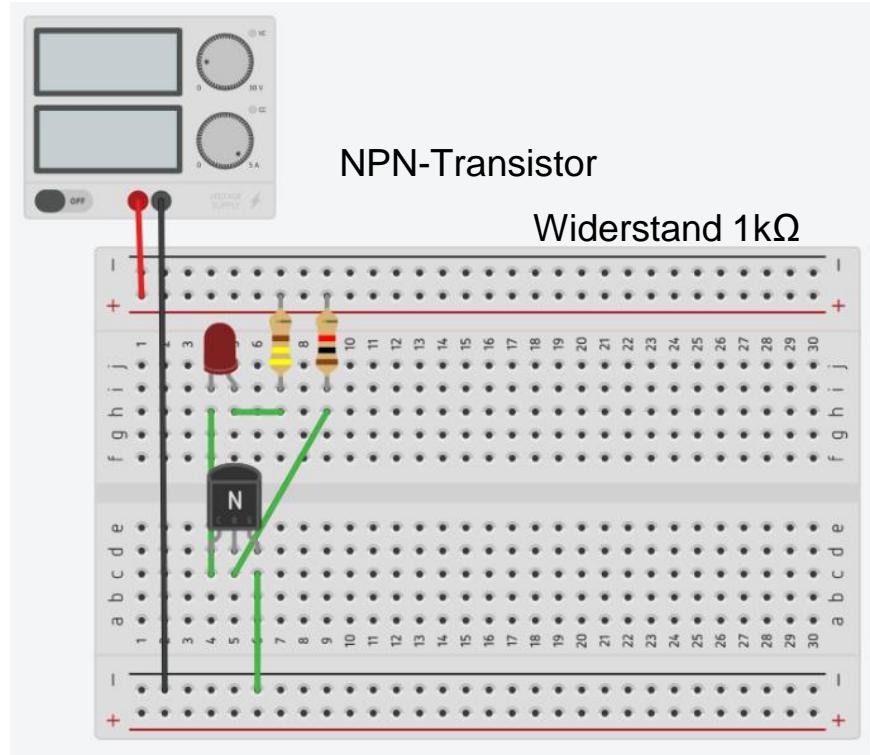

# Transistor


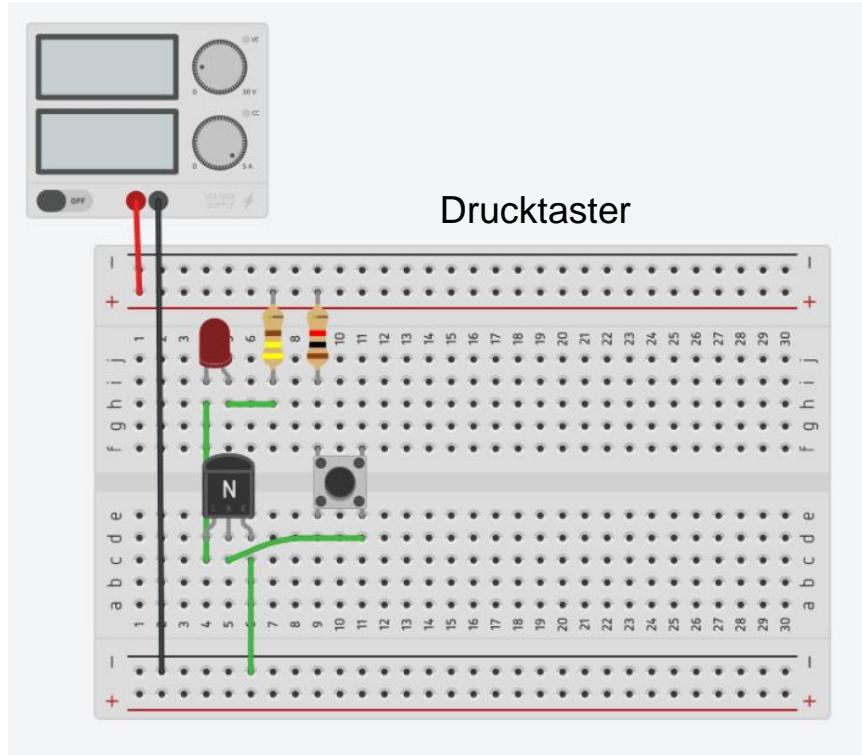


# AND-Gate

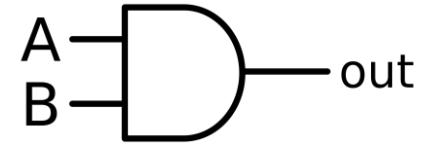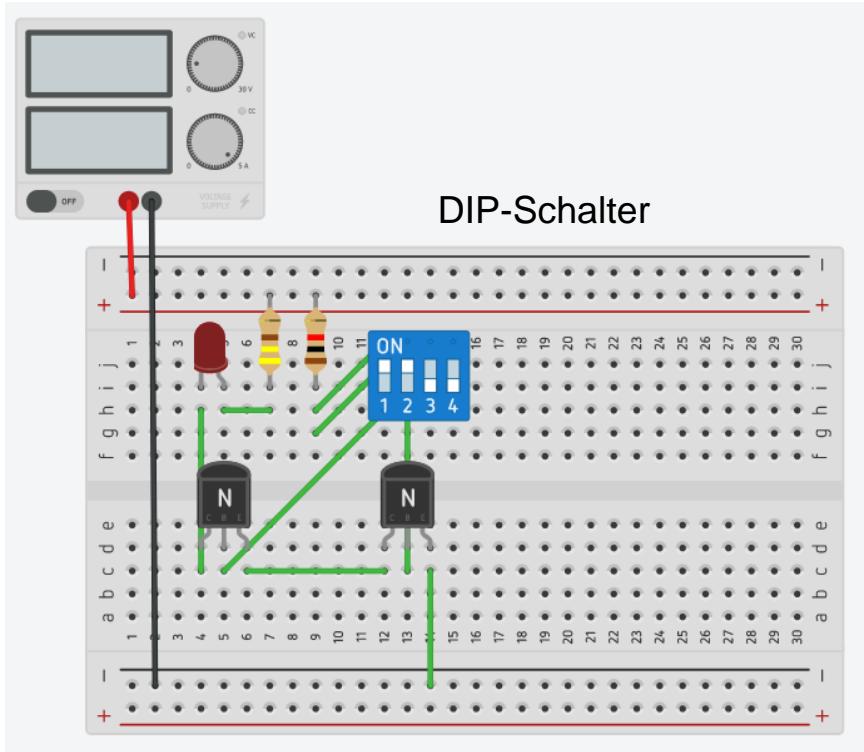







A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

# AND-Gate

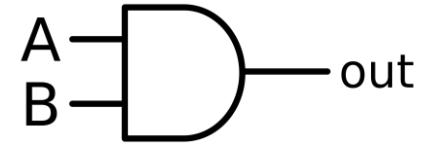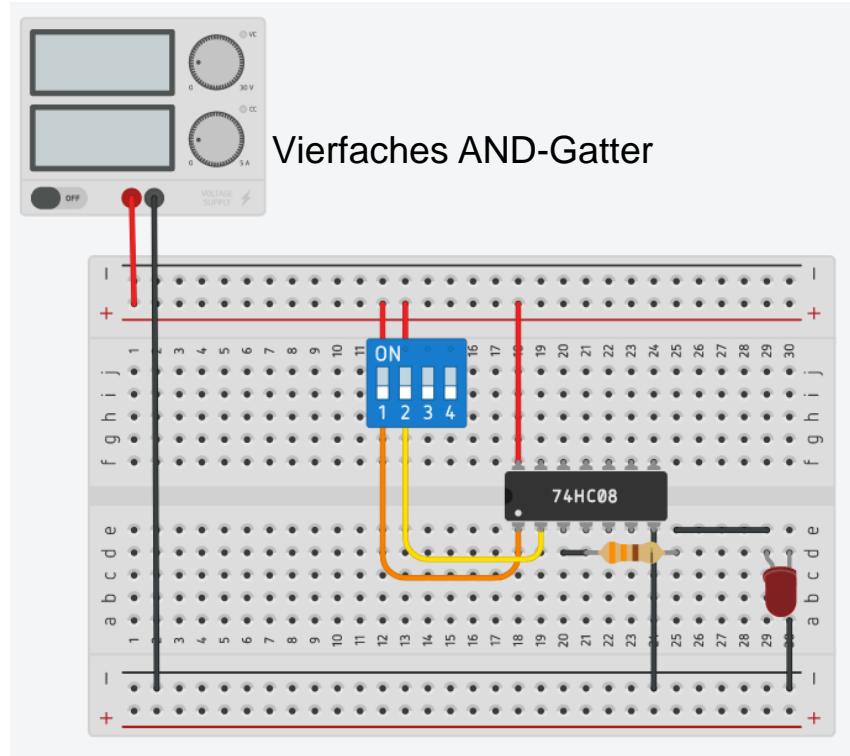


A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

# NAND, NOR, XOR, AND, OR, X

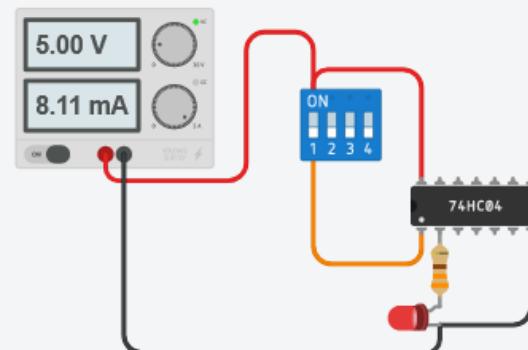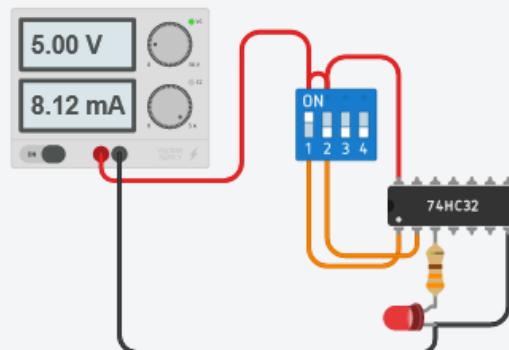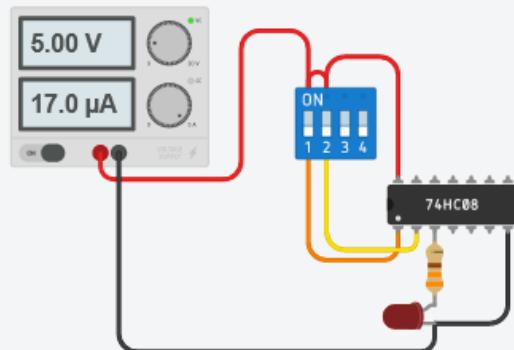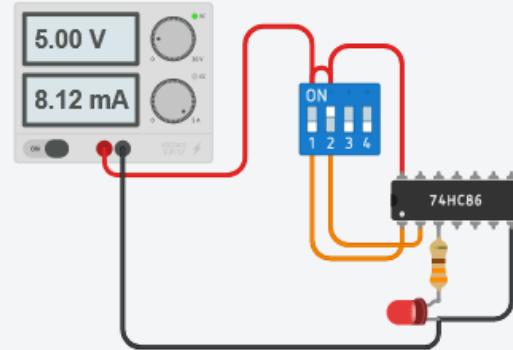
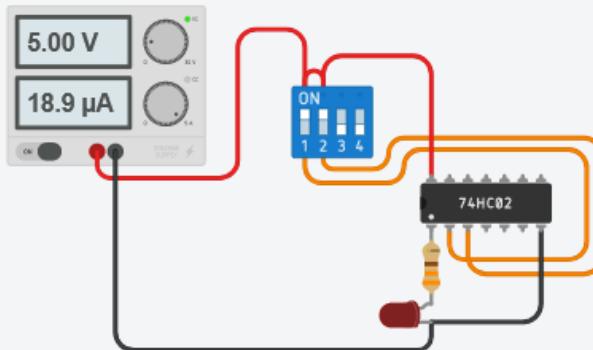
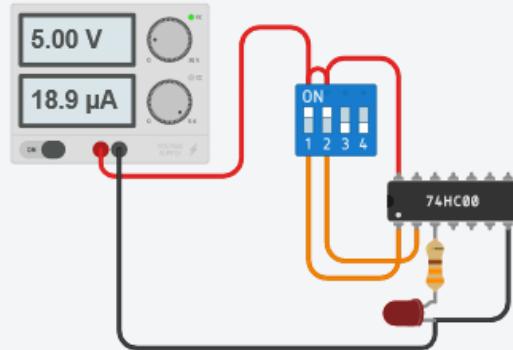


# Logic Gates

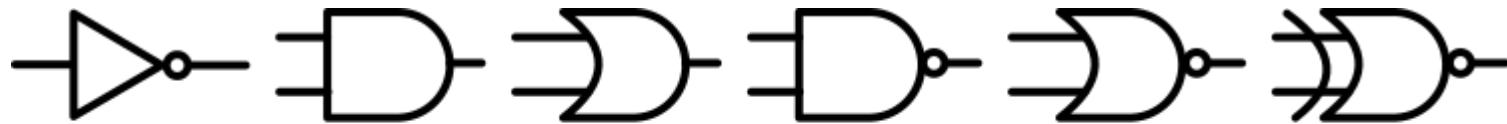


NOT    AND    OR    NAND    NOR    XOR

# Logic Gates as NAND

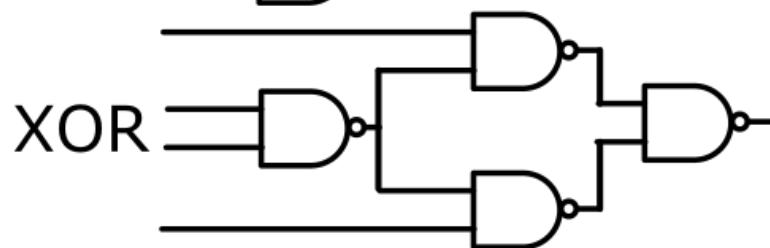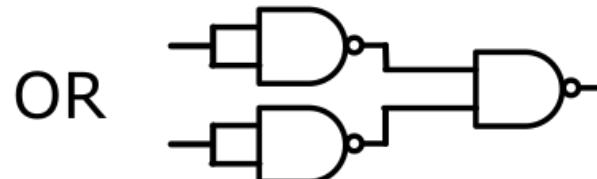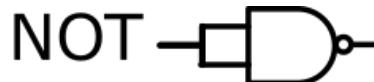


# Addierer


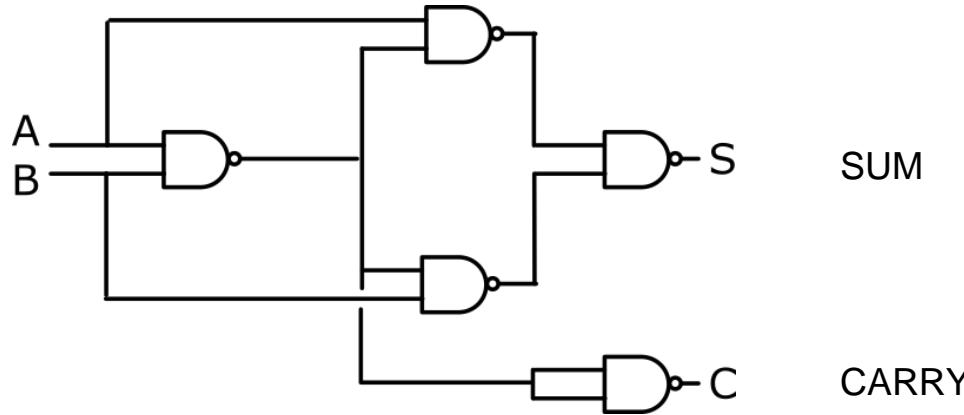


A+B	S	C
0+0	0	0
0+1	1	0
1+0	1	0
1+1	0	1

# Multiplizierer

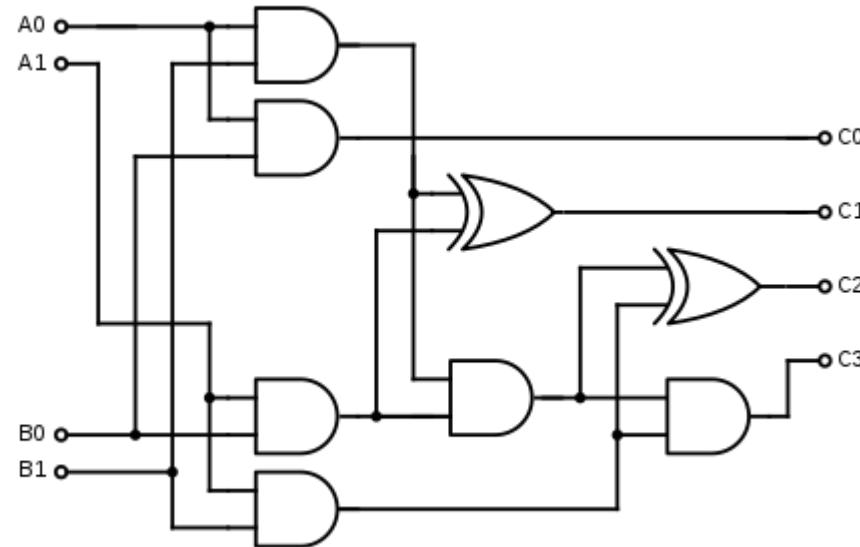

# Flip Flop

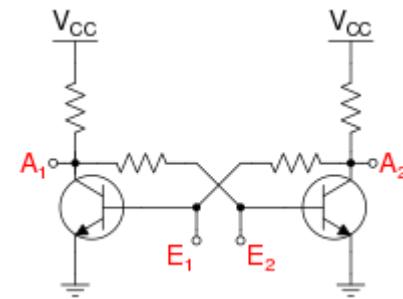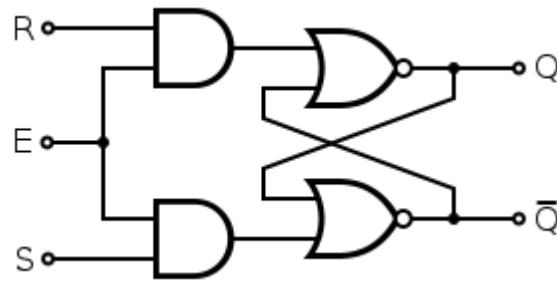


# Übung


Wie kann man die Dezimal-Binär Umwandlung am PC machen?

- Mit einer Tabellenkalkulation (Excel, Google Sheets, Open Office Calc, Numbers, etc.)
- (keine Umrechnungsfunktion nutzen, sondern “händisch”)
- 15 Minuten Zeit!

# Domino OR, XOR

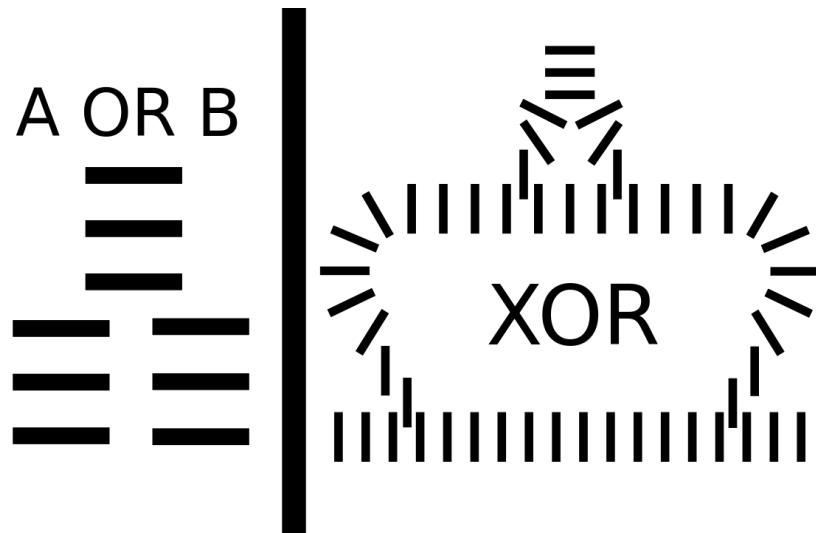


# Boolsche Algebra

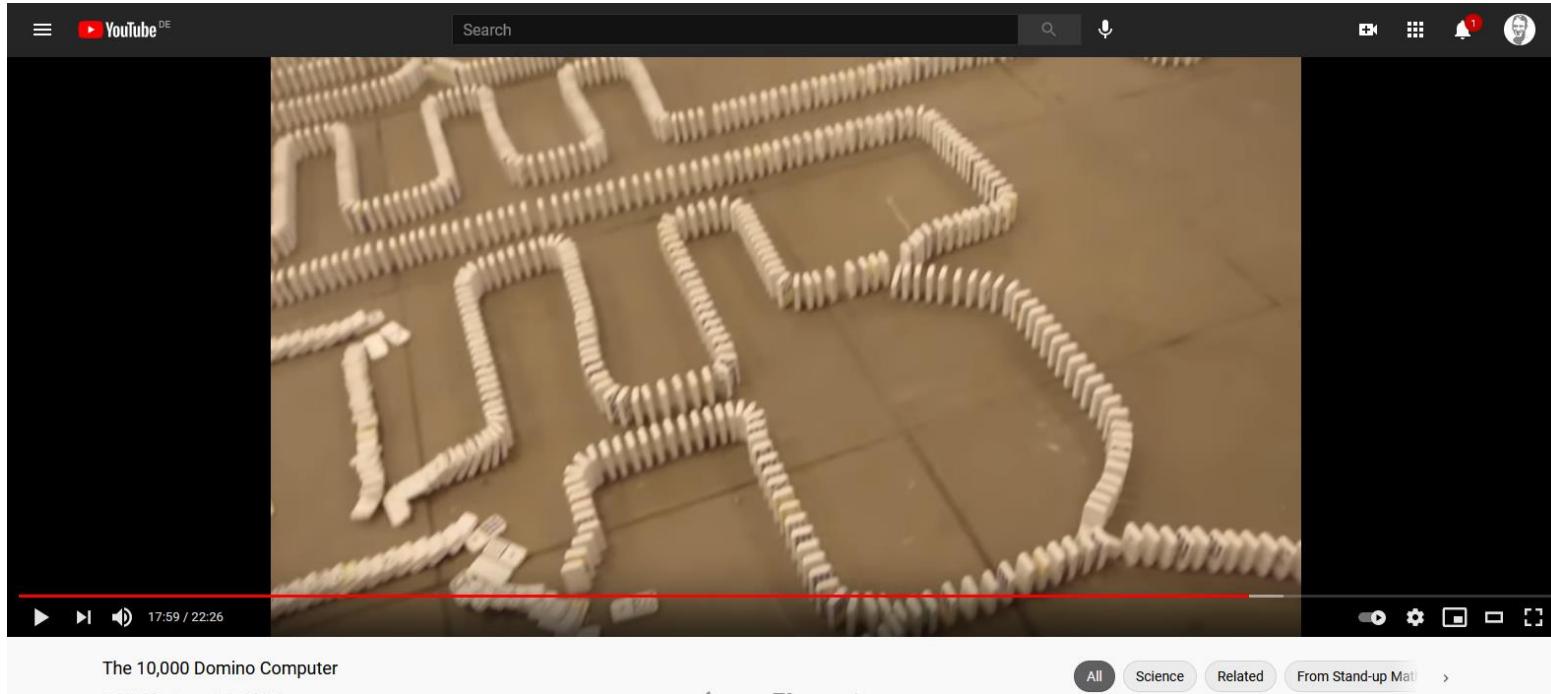

**Matt Parker: The 10,000 Domino Computer**

[https://youtu.be/OpLU\\_bhu2w](https://youtu.be/OpLU_bhu2w)

# Boolsche Algebra

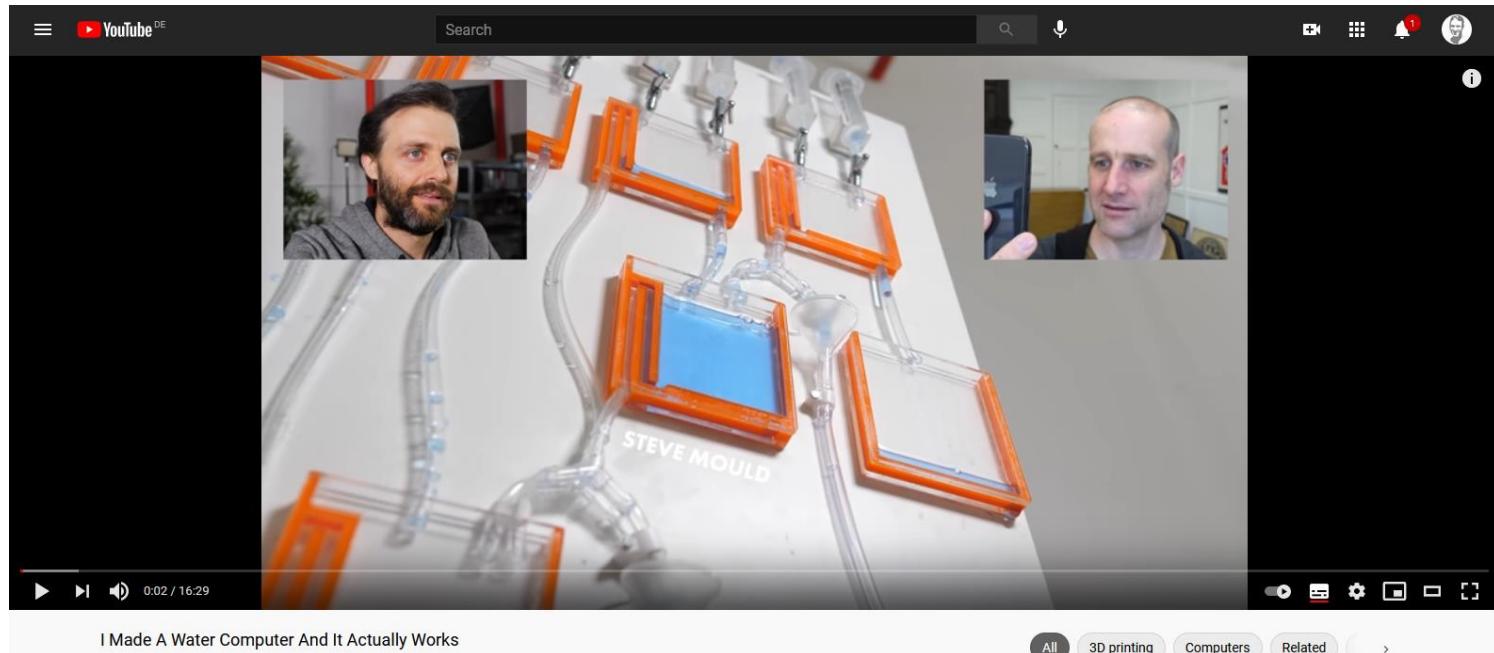

I Made A Water Computer And It Actually Works

All 3D printing Computers Related >

Steve Mould: I Made A Water Computer And It Actually Works

<https://youtu.be/IxXaizglscw>

# Boolsche Algebra



Minecraft - Programmable 8-bit Computer - YouTube


YouTube · Michael Roberts

<https://youtu.be/ydd6l3iYOZE>

<https://eater.net/8bit>

# Testat

# Binär-Zähler von 0-7

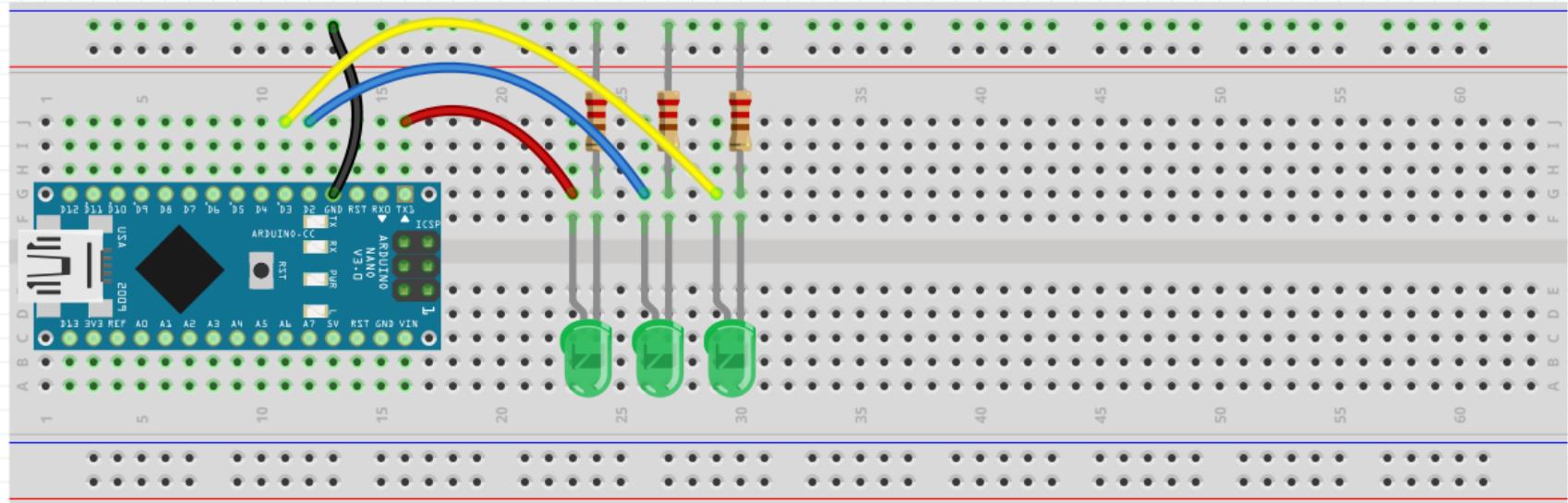

# Vielen Dank fürs Mitmachen!

Ferdinand Meier  
FME@hsrw.eu

Bis übernächste Woche!

